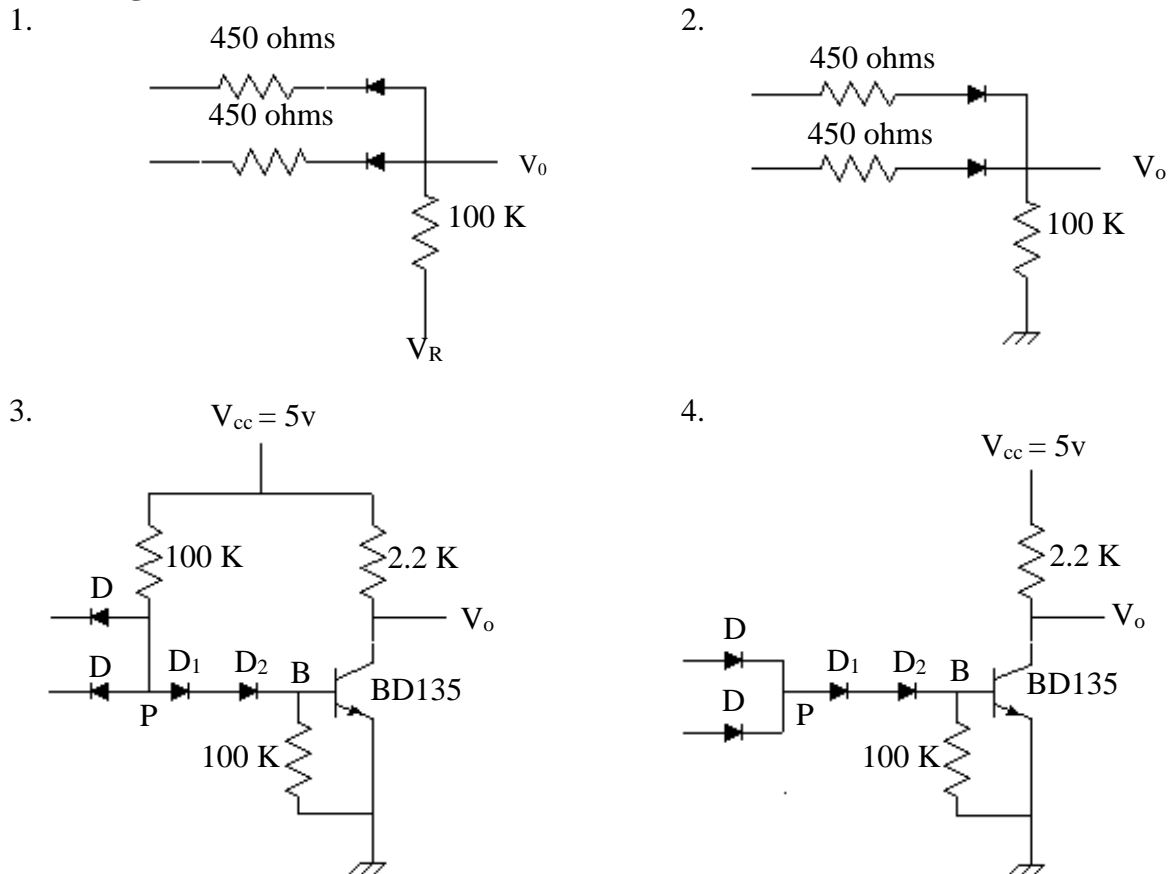


Experiment # 1

Name of the experiment: Study of DL and DTL gates.

CKT diagram:



Procedure:

1. For ckt1 and ckt2 measure the output voltage V_o for all possible input combinations.
2. For ckt3 and ckt4 measure V_D , V_{D1} , V_{D2} , V_P , V_{CE} and V_o for all possible inputs. Calculate the $h_{FE(min)}$, $NM(0)$ and $NM(1)$.

Questions:

1. Analyze the ckt1 and ckt2 with the help of truth table for both positive and negative logic. [ck1, ck2]
2. What happens in V_R is more positive than $V(1)$? [ck1]
3. What happens if not all inputs have the same upper level? [ck1, ck2]
4. Why diode D_2 is used? [ck3, ck4]
5. Can emitter and collector be interchanged? [ck3, ck4]
6. What is the significant of $h_{FE(min)}$? [ck3, ck4]


Report:

1. Objective.
2. Circuit diagram.
3. Answer to the questions.
4. Experimental data.
5. Calculations.
6. Discuss the findings.

Experiment #2

Name of the experiment: Study of a transistorized NOT gate.

CKT diagram:

 

Procedure:

1. Fix the value of R_1 , R_2 , V and vary R_3 ; measure V_0 and V_B .
2. Fix the value of R_1 , R_3 , V and vary R_2 ; measure V_0 and V_B .
3. Fix the value of R_2 , R_3 , V and vary R_1 ; measure V_0 and V_B .
4. Fix the value of R_1 , R_2 , R_3 and vary V ; measure V_0 and V_B .

Questions:

1. Which factor affect the switching speed of a transistor and how?
2. What is the effect of R_1 ? Can it be very large?
3. Are there any effects of temperature on the circuit?


Report:

1. Objective.
2. Circuit diagram.
3. Answer to the questions.
4. Experimental data.
5. Calculations.
6. Discuss the findings.

Experiment # 3

Name of the experiment: Study of a TTL NAND gate with totem-pole output.

Circuit Diagram:

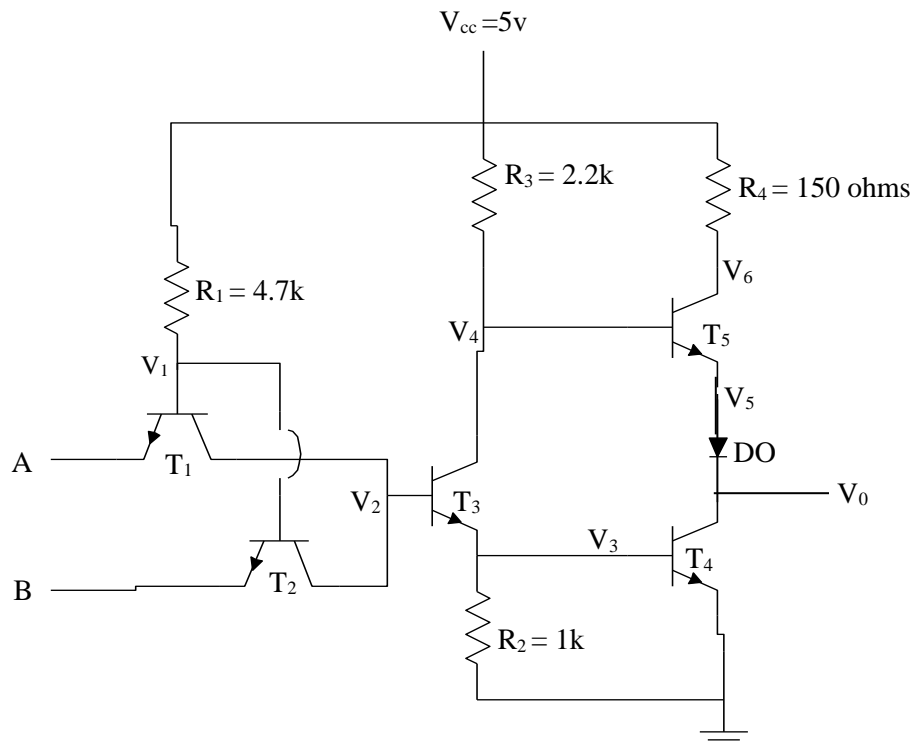

Procedure:

1. Measure the V_0 , V_1 , V_2 , V_3 , V_4 , V_5 & V_6 for all possible input combinations.
2. Calculate noise margins.

Questions:


1. Analyze the operation of TTL NAND gate with the experimental data.
2. What are the differences of transistors T_1 & T_2 with that of a multi-emitter transistor? [Hint: Millman Sec 4-7,5-11]
3. What is totem-pole stage? Why it is used in place of passive pull-up resistor? [Hint: Millman Sec 5-12]
4. What is the function of T_3 ? [Hint: Millman Sec 5-12]
5. Why resistor R_4 is used? [Hint: Millman Sec 5-12]
6. Why diode D_0 is used in the circuit? Can it be placed elsewhere? [Hint: Millman Sec 5-12]
7. Why two totem pole gates cannot be wire ANDed? [Hint: Millman pg. 151]
8. What are the features and advantages of TTL gates? [Hint: Millman Sec 5-15]

Report:

 1. Objective.
2. Circuit diagram.
3. Answer to the questions.
4. Experimental data.
5. Calculations.
6. Discuss the findings.

Experiment # 4

Name of the experiment: Study of a RTL NOR gate.



Procedure:

1. Measure the output voltage (V_o) for all possible input combinations.
2. Connect the V_{i1} input to ground, vary V_{i2} and measure V_o .
3. Connect the V_{i2} input to ground, vary V_{i1} and measure V_o .

Questions:

1. Analyze the operation of RTL NOR gate with the experimental data.
2. What is the importance of studying the RTL gate? [Hint: Millman pg. 162]
3. Draw the V_o vs. V_{i1} and V_{i2} curves.


Report:

1. Objective.
2. Circuit diagram
3. Answer to the questions.
4. Experimental data.
5. Calculations.
6. Discuss the findings.

Experiment # 5

Name of the Experiment: Implementation of clocked SR Flip Flop using RTL NOR gates.

Circuit Diagram:

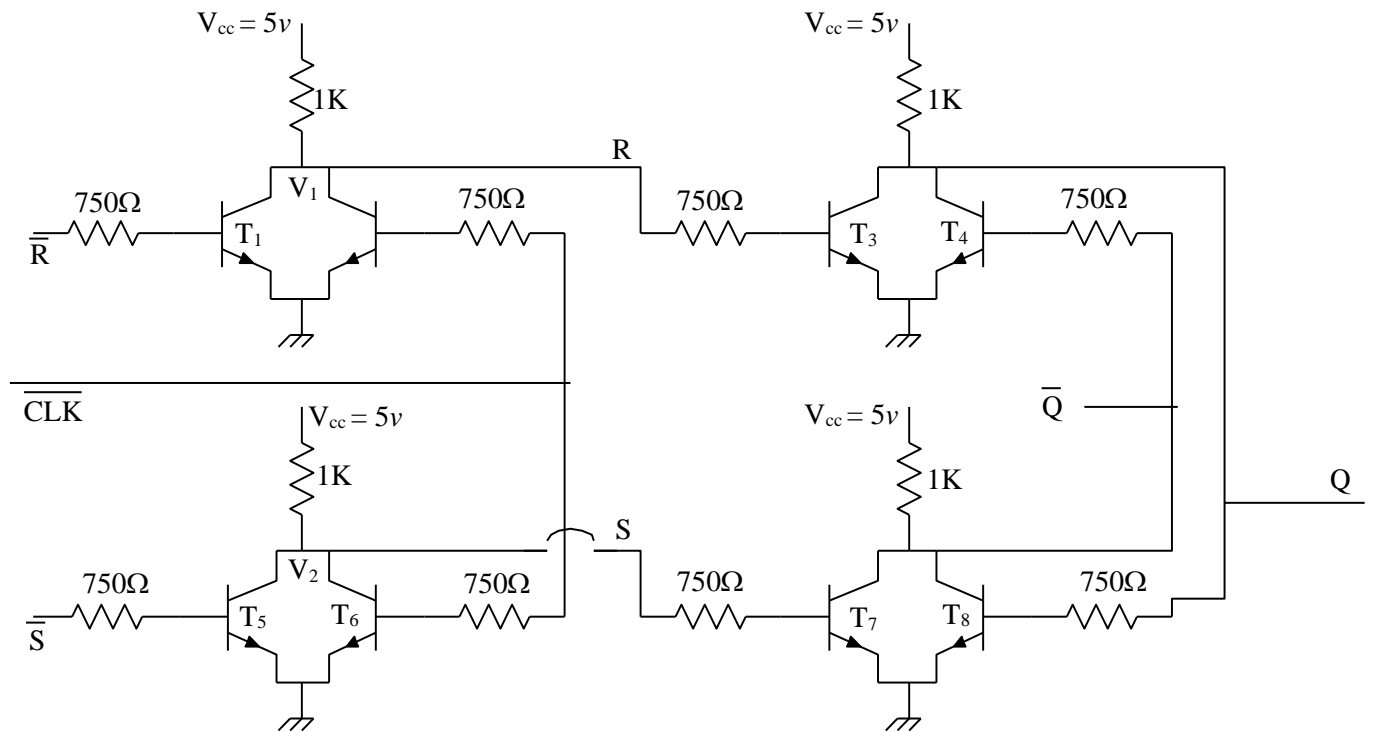

Procedure:

1. Measure the output voltages at Q & \bar{Q} and voltages V₁, V₂ for all possible input (S,R) combinations.

Questions:

1. Analyze the operation of SR FF with the experimental data.
2. What is the race around condition in SR FF? Discuss with respect to the internal circuit.

Report:

1. Objective.
2. Circuit diagram.
3. Answer to the questions.
4. Experimental data.
5. Calculations.
6. Discuss the findings.